




# Лингвистические средства проектирования

The screenshot displays a VHDL editor interface. At the top, there are tabs for 'counter.vhd', 'example\_vhd1.vhd', 'example\_vhd2.vhd', and 'example\_vhd3.vhd'. The main window shows a timing diagram for a signal 'kate' with a period of 10 units. Below the timing diagram, there is a VHDL code snippet for an entity named 'counter'. The code includes a generic parameter 'n' set to 2, and ports for 'clock', 'clear', 'count', and 'Q'. The code also includes library declarations for 'ieee.std\_logic\_1164.all' and 'ieee.std\_logic\_unsigned.all'. Below the code, there are two logic circuit diagrams. The first diagram shows a full adder circuit with inputs A and B, and outputs A+B and (A+B)(AB). The second diagram shows a full subtractor circuit with inputs A and B, and outputs A-B and (A+B)(AB).

Лекция 2

Основы описания структурного, регистрового и поведенческого архитектурных тел.

# Архитектура проекта на VHDL

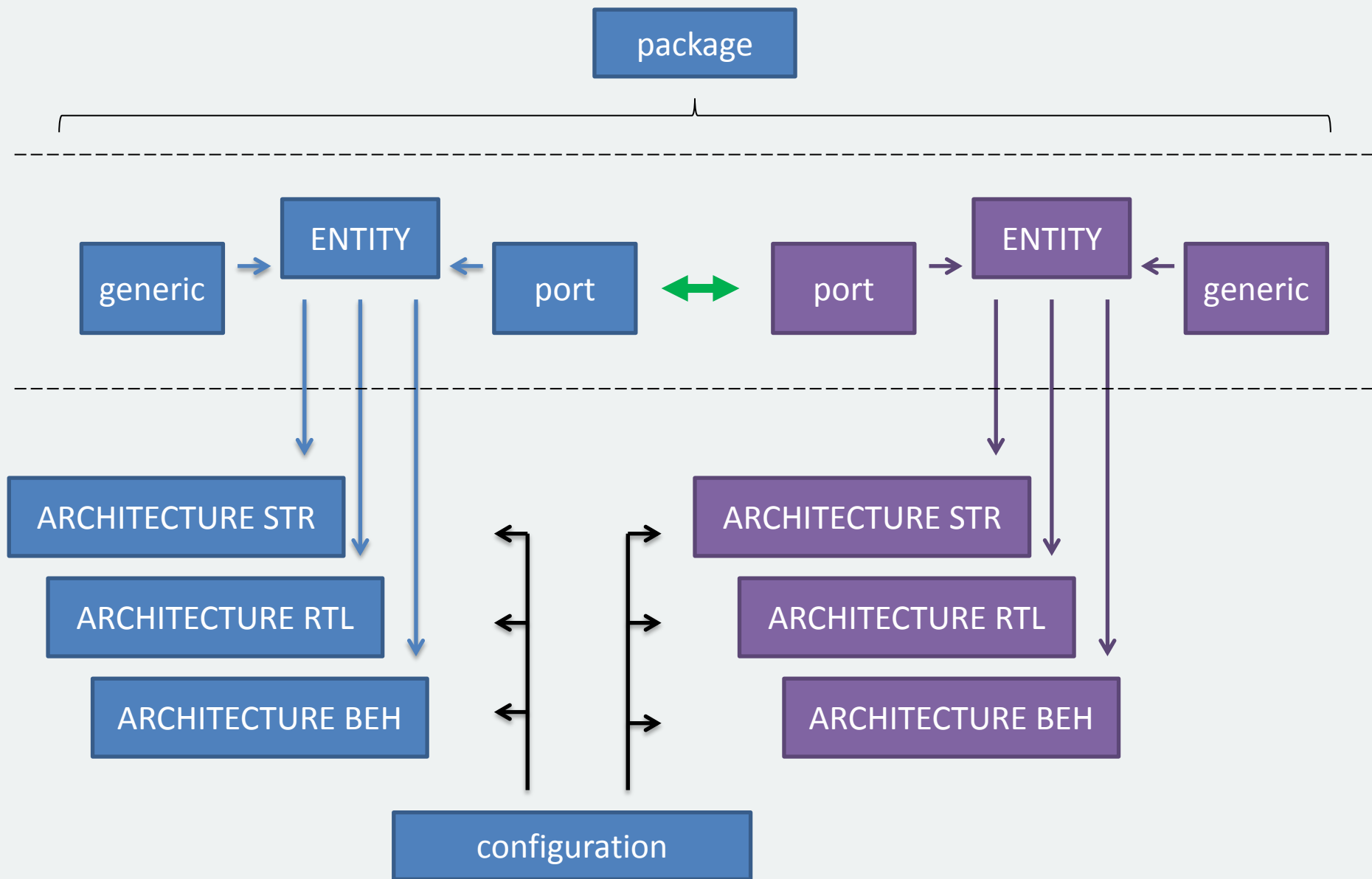



## Интерфейс устройства

```
entity <имя_интерфейса> is  
  
    [ generic (<список_параметров>) ; ]  
    [ port (<список_портов>) ; ]  
  
    [ begin  
  
        <типы данных, значения констант>;  
  
    ]  
  
end [entity] [<имя_интерфейса>];
```



## Архитектура устройства

**architecture** <имя\_архитектуры> **of** <имя\_интерфейса> **is**

[<список\_объявлений>; ]

**begin**

<список\_параллельных\_операторов>;

**end** [**architecture**] [<имя\_архитектуры>; ]

# Операторы языка VHDL для описания RTL

## NOT

x	y
0	1
1	0

## NAND

x1	x2	y
0	0	1
0	1	1
1	0	1
1	1	0

## NOR

x1	x2	y
0	0	1
0	1	0
1	0	0
1	1	0

## XOR

x1	x2	y
0	0	0
0	1	1
1	0	1
1	1	0

## AND

x1	x2	y
0	0	0
0	1	0
1	0	0
1	1	1

## OR

x1	x2	y
0	0	0
0	1	1
1	0	1
1	1	1


## XNOR

x1	x2	y
0	0	1
0	1	0
1	0	0
1	1	1
 
## Элемент «исключающее или» (1)


```
entity xor2 is
  port (x1, x2: in std_logic;
        y: out std_logic);
end xor2;
```

```
architecture RTL of xor2 is
begin
  y <= x1 xor x2;
end RTL;
```


 
## Элемент «исключающее или» (2)

```
entity xor2 is
  port (x1, x2: in std_logic;
        y: out std_logic);
end xor2;
```




```
architecture RTL of xor2 is
begin
  y <= (x1 and (not x2)) or ((not x1) and x2);
end RTL;
```

## Структурное архитектурное тело

**Структурное архитектурное тело** описывает поведение схемы косвенно, через поведение компонентов.

```
entity DEVICE is  
  port (...);  
end DEVICE;
```
 
```
architecture STR of DEVICE is  
  ...  
begin  
  ...  
end STR;
```






## Пример. Этап 1: проектирование библиотеки

```
entity inv is
  port(x: in bit;
        y: out bit);
end inv;
```

```
architecture RTL of inv is
begin
  y <= not x;
end RTL;
```


+ тестбенч

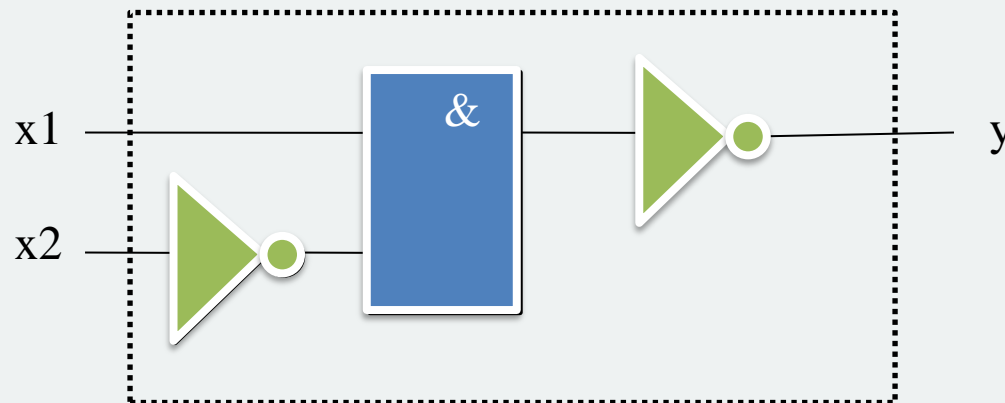



```
entity and2 is
  port(x1, x2: in bit;
        y: out bit);
end and2;
```

```
architecture RTL of and2 is
begin
  y <= x1 and x2;
end RTL;
```

+ тестбенч

 

  
## Пример. Этап 2: описание интерфейса схемы



```
entity DEVICE is  
    port (x1: in bit;  
          x2: in bit;  
          y: out bit);  
end DEVICE;
```
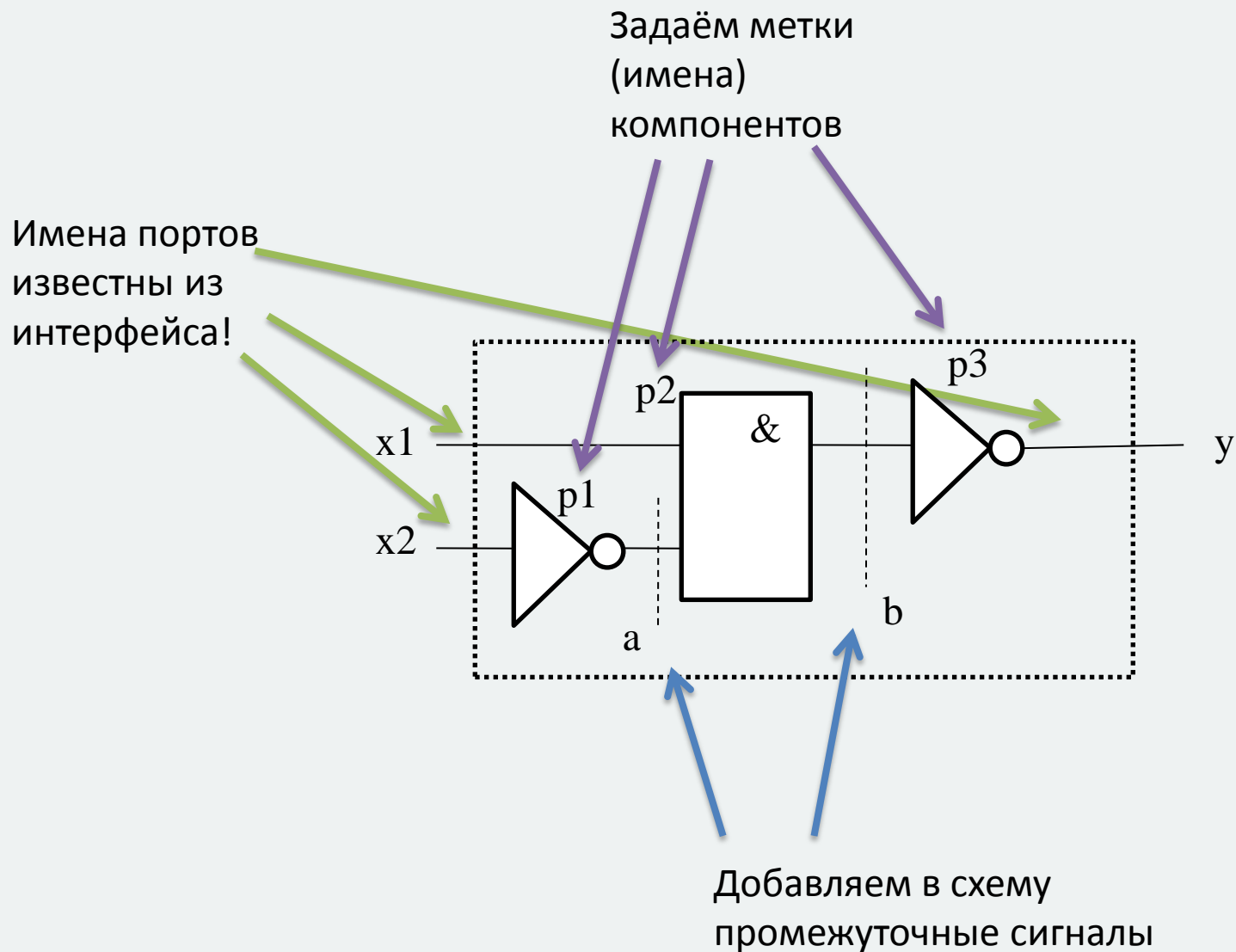
## Пример. Этап 3: расстановка недостающих объектов



## Пример. Этап 4: описание взаимосвязи компонентов


```
architecture STR of DEVICE is
  component inv
    port (x: in bit; y: out bit);
  end component;
  component and2
    port (x1, x2: in bit; y: out bit);
```

```
  signal a, b: bit;
```

```
begin
```

```
  p1 : inv port map (x2, a);
  p2 : and2 port map (x1, a, b);
  p3 : inv port map (b, y);
```

```
end STR;
```

 

Какие типы элементов  
будут использованы?

Перечень недостающих  
сигналов

Связь элементов  
посредством сигналов и  
портов

## Ассоциативное описание портов


```
architecture STR of DEVICE is
  ...
  component inv
    port(y: out bit; x: in bit);
  end component;
  ...
begin
  p1 : inv port map(x2, a);
  ...
end;
```



```
p1 : inv port map(x2, a);

p2 : and2 port map(x1, a, b);


p3 : inv port map(b, y);
```

 

```
p1 : inv port map(x=>x2, y=>a);

p2 : and2 port map(x1=>x1, x2=>a, y=>b);

p3 : inv port map(y=>y, x=>b);
```

 

## Использование настраиваемых параметров (2)

Задержка указывается с помощью настраиваемого параметра

```
entity inv is
  generic (t: time);
  port (x: in bit;
        y: out bit);
end inv;
```

```
architecture RTL of inv is
begin
```

```
  y <= not x after t;
end RTL;
```


```
entity <имя_интерфейса> is
```

```
  [ generic (<список_параметров>); ]
```

```
  [ port (<список_портов>); ]
```

```
end [entity] [<имя_интерфейса>];
```
 
## Использование настраиваемых параметров



```
p1 : inv port map(x, a);
```

```
p2 : inv port map(a, b);
```

```
p3 : inv port map(b, y);
```

```
p1 : inv port map(x, a)  
→ generic map(4 ns);
```

```
p2 : inv port map(a, b)  
→ generic map(3.8 ns);
```

```
p3 : inv port map(b, y)  
→ generic map(3.6 ns);
```


```
entity <имя_интерфейса> is
```

```
→ [ generic(<список_параметров>); ]
```

```
[ port(<список_портов>); ]
```

```
end [entity] [<имя_интерфейса>;
```

## RTL-описание схем

 

```
entity DEVICE is
  port(x1: in bit;
        x2: in bit;
        y: out bit);
end DEVICE;
```


```
architecture STR of DEVICE is
  component inv
    port(x: in bit; y: out bit);
  end component;
  component and2
    port(x1, x2: in bit; y: out bit);
  end component;
```

```
signal a, b: bit;
```

```
begin
```

```
p1 : inv port map(x2, a);
p2 : and2 port map(x1, a, b);
p3 : inv port map(b, y);
```

```
end STR;
```

 

```
architecture RTL of DEVICE is
```

```
signal a, b: bit;
```

```
begin
```

```
p1 : a <= not x2;
p2 : b <= a and x1;
p3 : y <= not b;
```

```
end RTL;
```



 
## Формы RTL-описания схем


```
architecture RTL of DEVICE is
  signal a, b: bit;
begin
  p1 : a <= not x2;
  p2 : b <= a and x1;
  p3 : y <= not b;
end RTL;
```



```
architecture RTL of DEVICE is
begin
  p1 : y <= not (x1 and not x2);
end RTL;
```


 
```
architecture RTL of DEVICE is
begin
  p1 : y <= x1 nand (not x2);
end RTL;
```



## Комбинирование описаний сложных схем


```
architecture STR of DEVICE is
  component and2
    port(x1, x2: in bit; y: out bit);
  end component;

  signal a, b: bit;
begin

  p1 : a <= not x2;
  p2 : y <= not b;


  p3 : and2 port map(x1, a, b);

end STR;
```

 

## Поведенческое архитектурное тело

x1	x2	y
0	0	1
0	1	1
1	0	0
1	1	1

 

```
entity DEVICE is
  port(x1: in bit;
        x2: in bit;
        y: out bit);
end DEVICE;
```

```
architecture BEH of DEVICE is
begin
  process(x1, x2)
  begin
    if(x1='1' and x2='0') then
      y <= '0';
    else
      y <= '1';
    end if;
  end process;
end BEH;
```


## Описание тестовых последовательностей с помощью процессов

```
signal x : std_logic;
```

```
...
```

```
p1 : x <= '0' after 0 ns, '1' after 10ns, '0' after 20 ns,
```

```
...
```

 

```
signal x : std_logic;
```

```
...
```

```
p1 : process  
begin  
    x <= '0';  
    wait for 10 ns;  
    x <= '1';  
    wait for 10 ns;  
end process;
```