



Лингвистические средства проектирования

The screenshot displays a VHDL editor window with a file explorer at the top showing 'counter.vhd', 'example_vhd1.vhd', 'example_vhd2.vhd', and 'example_vhd3.vhd'. The main window shows a timing diagram for a clock signal 'kate' and a VHDL code snippet for an entity 'counter'. Below the code, a logic circuit diagram is shown, illustrating the implementation of a counter using logic gates and flip-flops. The circuit includes inputs A and B, and outputs A+B and A⊕B. The code defines a generic counter with a clock, clear, and count input, and a Q output vector.

```
entity counter is
  generic (n : natural := 2);
  port (
    clock : in std_logic;
    clear : in std_logic;
    count : in std_logic;
    Q : out std_logic_vector(n-1 downto 0)
  );
end counter;
```

Лекция 3

Поведенческое архитектурное тело



Процессы – строительные блоки поведенческого описания

[<метка>:] **process** [(<сигналы>)] [**is**]

[объявления]

begin

[последовательные операторы]

end [process] [<метка>];

architecture ВЕН **of** DEVICE **is**

...

begin

p1 : **process** (x1, a1)
 begin

...

end process;

p2 : **process** (x2, a2, c)
 begin

...

end process;

...


end ВЕН;

Формы описания процессов

В процессе обязана быть одна из двух конструкций:

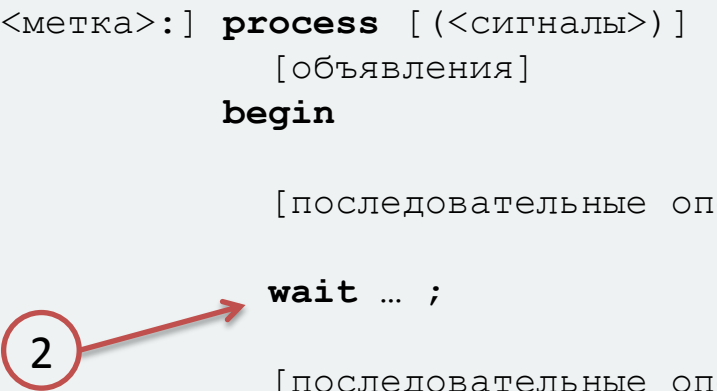1. список чувствительности;
2. оператор ожидания.

```
[<метка>:] process [ (<сигналы> ) ] [is]  
           [объявления]  
begin  
  
           [последовательные операторы]  
  
           wait ... ;  
  
           [последовательные операторы]  
  
end [process] [<метка>];
```




Без списка чувствительности процесс работает **бесконечно** переходя от одной итерации к другой.

Если процесс не содержит ни списка чувствительности, ни оператора ожидания, он **входит в закливание, моделирование становится невозможным.**

Поведенческое архитектурное тело

x1	x2	y
0	0	1
0	1	1
1	0	0
1	1	1

 

```
entity DEVICE is
  port(x1: in bit;
        x2: in bit;
        y: out bit);
end DEVICE;
```

```
architecture BEH of DEVICE is
begin
  process(x1, x2)
  begin
    if(x1='1' and x2='0') then
      y <= '0';
    else
      y <= '1';
    end if;
  end process;
end BEH;
```

Формы записи оператора wait

wait – оператор ожидания.

4 формы записи оператора:

1. ожидание в течение определённого времени;

```
wait for <время>;
```

2. ожидание изменения сигнала;

```
wait on <список_сигналов>;
```

3. ожидание выполнения логического условия,

```
wait until <логическое_условие>;
```

4. остановка процесса.

```
wait;
```


Ожидание в течение заданного времени

x : 

p1: x <= '1' **after** 0 ns, '0' **after** 20 ns, '1' **after** 40 ns, ...


 
```
p1 : process
  begin
    x <= '1';
    wait for 20 ns;
    x <= '0';
    wait for 20 ns;
  end process;
```



```
p1 : process
  begin
    x <= not x;
    wait for 20 ns;
  end process;
```



Правильное использование начальных значений сигналов

```
architecture TEST of tb_dctt is
  component dctt
    port(d, c: in std_logic;
         q, nq: out std_logic);
  end component;

  signal d, c: std_logic := '0';
  signal q, nq: std_logic;

begin
  p1 : dctt port map(d, c, q, nq);

  p2 : process
    begin
      c <= not c;
      wait for 7ns;
    end process;

  p3 : process
    begin
      d <= not d;
      wait for 19ns;
    end process;
end BEH;
```

Покрытие набора входных воздействий

AND2

x2	x1	y
0	0	0
0	1	0
1	0	0
1	1	1

```
p1 : process
begin
    wait for 10 ns;
    x1 <= not x1;
end process;
```

```
p2 : process
begin
    wait for 20 ns;
    x2 <= not x2;
end process;
```

```
p1 : process
begin
    wait for 10 ns;
    x1 <= not x1;
end process;
```

```
p2 : process
begin
    wait on x1;
    wait on x1;
    x2 <= not x2;
end process;
```




Ожидание логического условия

AND2

x2	x1	y
0	0	0
0	1	0
1	0	0
1	1	1

```
p1 : process
begin
    wait for 10 ns;
    x1 <= not x1;
end process;
```

```
p2 : process
begin
    wait for 20 ns;
    x2 <= not x2;
end process;
```

```
p1 : process
begin
    wait for 10 ns;
    x1 <= not x1;
end process;


p2 : process
begin
    wait until x1 = '0';
    x2 <= not x2;
end process;
```




Остановка процесса

```
p1 : disable <= '0', '1' after 150 ns, '0' after 160 ns;
```
 
```
p2 : process  
  begin  
    x <= not x;  
    wait for 5 ns;  
    if(disable = '1') then  
      wait;  
    end if;  
  end process;
```



Константы, переменные, сигналы

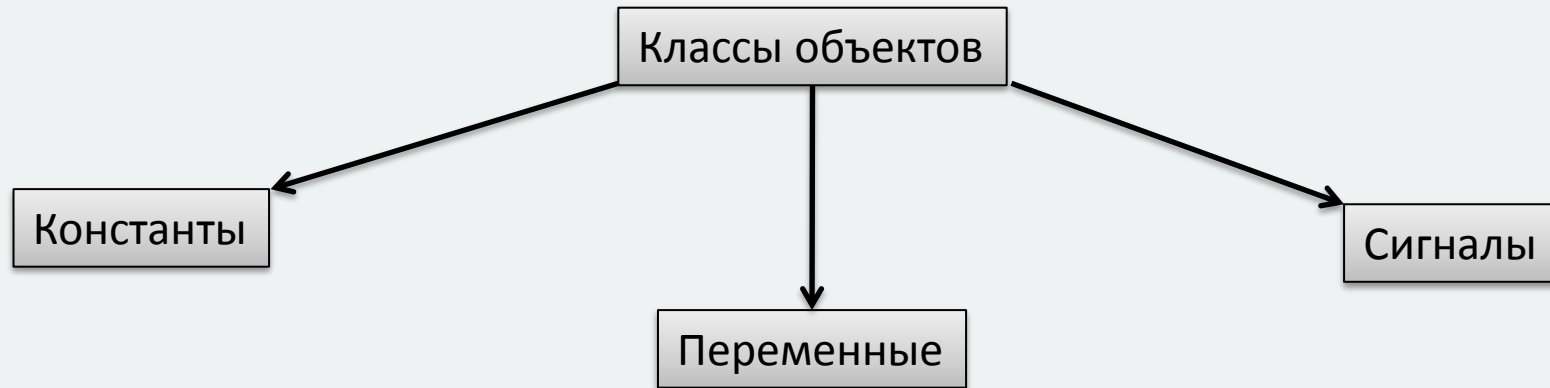

```
constant LOGIC_ONE : std_logic := '1';
```


```
variable TEMP_VAR : std_logic := '1';
```

```
signal CONNECT : std_logic := '1';
```

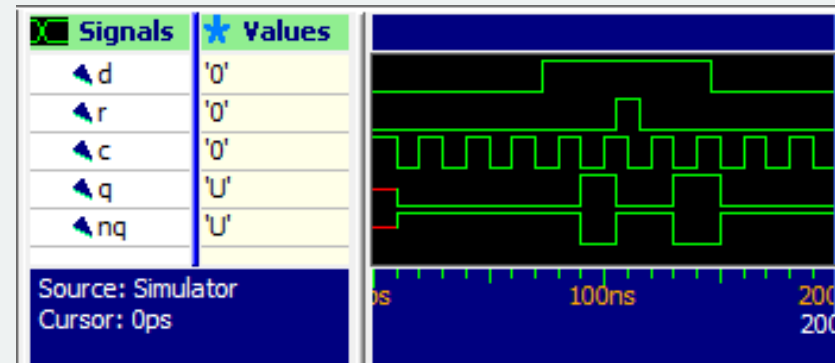Пример использования переменных

```
entity DCTT is  
  port(D, C, R: in std_logic;  
        Q, nQ  : out std_logic);  
end DCTT;
```

```
architecture BEH of DCTT is  
begin  
  p1: process(C, R)  
    variable temp : std_logic;  
  begin  
    if(R = '1') then  
      temp := '0';  
    else  
      if(C = '0' and not C'stable) then  
        temp := D;  
      end if;  
    end if;  
    Q <= temp;  
    nQ <= not temp;  
  end process;  
end BEH;
```



Атрибуты сигналов

Имя атрибута	Назначение атрибута, что возвращает
<code>S' stable,</code> <code>S' stable (T)</code>	true, если сигнал не менялся (в течение времени T)
<code>S' event</code>	true, если происходит изменение сигнала
<code>S' active</code>	true, если была запись, но значение ещё не поменялось
<code>S' quiet (T)</code>	true, если не было обращений в течение времени T
<code>S' last_value</code>	предыдущее значение сигнала
<code>S' last_event</code>	время предыдущего изменения сигнала



Определение фронта сигнала

```
process (C)
begin
  if (not C'stable and C='1') then
    ...
```

```
process (C)
begin
  if (C'event and C='1') then
    ...
```

```
library ieee;
use ieee.std_logic_1164.all;
```

```
process (C)
begin
  if rising_edge(C) then
    ...
```



Условный оператор if


```
process (x1, x2)
begin
  if (x1 = '0' and x2 = '0') then
    y <= '0';
  elsif (x1 = '0' and x2 = '1') then
    y <= '1';
  elsif (...
    ...
  else
    ...
  end if;
end process;
```

XOR

x1	x2	y
0	0	0
0	1	1
1	0	1
1	1	0

```
process (x1, x2)
begin
  if (x1 /= x2) then
    y <= '1';
  else
    y <= '0';
  end if;
end process;
```

Оператор множественного выбора case

 

Тип данных: STD_LOGIC

R	S	Q	nQ
1	0	0	1
0	1	1	0
0	0	хранение	
1	1	запрещено	

```
process (R, S)
    variable RS: std_logic_vector(1 to 2);
begin
    RS := R & S;
    case RS is
        when "10" => Q <= '0';
                    nQ <= '1';
        when "01" => Q <= '1';
                    nQ <= '0';
        when "11" => Q <= 'X';
                    nQ <= 'X';
    end case;
end process;
```


Оператор NULL

Error: CSVHDL0139: test.vhdl: (line 14):

The number of choices for type "std_logic_vector(1 TO 2)" must be '81'.

Only '3' choice(s) given. Hint. Use OTHERS to specify missing choice(s)

```
process (R, S)
  variable RS: std_logic_vector(1 to 2);
begin
  RS := R & S;
  case RS is
    when "10" => Q <= '0';
                nQ <= '1';
    when "01" => Q <= '1';
                nQ <= '0';
    when "11" => Q <= 'X';
                nQ <= 'X';
    when others => NULL;
  end case;
end process;
```

